 


2.1 It give the same result because both code describe a module that function the same.


4.1 ShiftA both  $q[0]$  and  $q[1]$  will have the value of  $d$  when the positive edge of clock happen but shiftB  $q[0]$  will have the value of  $d$  and  $q[1]$  will also have the value of  $q[0]$  when the positive edge of clock happen

5.1 :

ShiftA :



ShiftB :

 

5.2: In the always block the blocking assignment ( $=$ ) is executed in series so the result we get will be depending on the sequence of the instruction but the non-blocking assignment ( $<=$ ) is executed in parallel so that the value that we assign to our register will be assigned to the register simultaneously at the end of the processing.

### 5.3: Yes by using Parameter

```
) module N_bit_Shift
  #(
    parameter N = 2
  )
  (
    output reg [N-1:0] q,
    input wire clock,
    input wire d
  );
  always @(posedge clock) begin
    q[N-1:1] <= q[N-2:0];
    q[0] <= d;
  end
endmodule
```

We can access this module by

```
N_bit_Shift #(.N(4)) u1(q, clock, d);
```

\*this is a 4 bit shif register\*