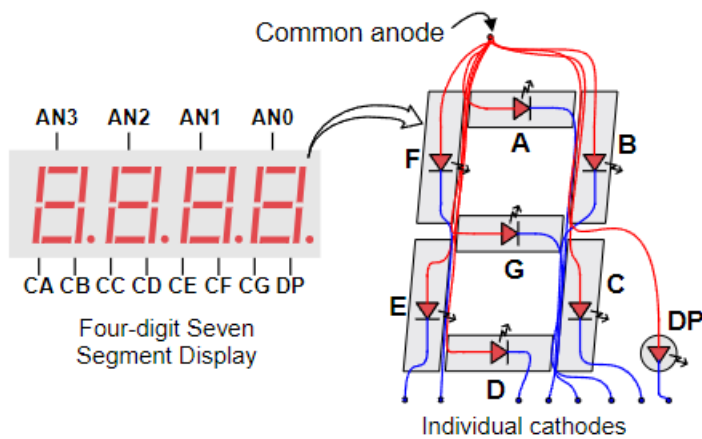


2.a: A common Anode because the anode of all the LED in Seven Segment Display is tied together as show in the picture below



2.b: the logic 0 will turn the LED on.

2.c: the clock time period is 10ns so it's frequency is $10/(10^{-9}) = 10^8$ HZ

For our LED to work the basys 3 manual recommend that the frequency is between 60 to 1000 HZ And each of the bit we add to the ClockDivider will divide the clock frequency by 2 time

So we get that $\log((10^7)/6) \geq$ the bit we need $\geq \log(10^5)$; for log is a log base 2

From calculation we get $20.67 \geq$ the bit we need ≥ 16.61 ; but the bit we need is an integer

So, we must round up thus we get $20 \geq$ the bit we need ≥ 17

ANS the bit we need must be in range of 17 to 20.